

Low Jun Jie 2002736

Ngo Bing Hun 2002814

Khin Kim Hong 1415249

EDS Student Design board

Date

No.

A-win = 8

B-win = 2

S/N	D	C	B	A	A-win	B-win	Decimal
1	0	0	0	0	x	x	0
2	0	0	0	1	x	x	1
3	0	0	1	0	0	1	2
4	0	0	1	1	0	0	3
5	0	1	0	0	0	0	4
6	0	1	0	1	0	0	5
7	0	1	1	0	0	0	6
8	0	1	1	1	0	0	7
9	1	0	0	0	1	0	8
10	1	0	0	1	x	x	9
11	1	0	1	0	x	x	10
12	1	0	1	1	x	x	11
13	1	1	0	0	x	x	12
14	1	1	0	1	x	x	13
15	1	1	1	0	x	x	14
16	1	1	1	1	x	x	15

A-win = 8

$\bar{B}\bar{A}$   $\bar{B}A$   $B\bar{A}$   $BA$

$\bar{D}\bar{C}$  x x 0 0

$\bar{D}C$  0 0 0 0

$\bar{D}\bar{C}$  (x x x x)

$D\bar{C}$  (1 x x x)

B-win = 2

$\bar{B}\bar{A}$   $\bar{B}A$   $B\bar{A}$   $BA$

$\bar{D}\bar{C}$  x x 0 V

$\bar{D}C$  0 0 0 0

$D\bar{C}$  x x x x

$DC$  0 x x (x)


A-win = 0

B-win =  $B\bar{A}\bar{C}$


For B-win

$$B\bar{A}\bar{C} = (\bar{A} + \bar{C}) \cdot B$$

To implement AND gate using NOR gate

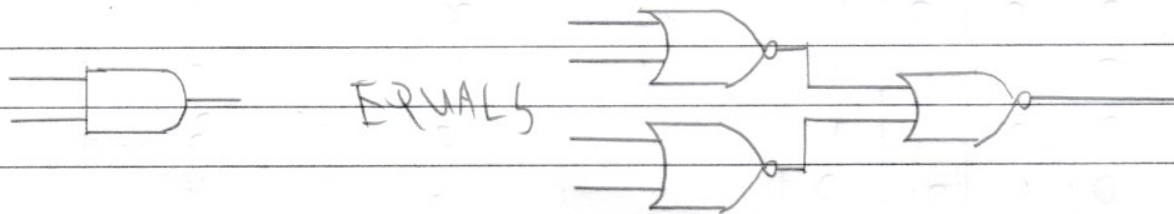

Implementing B-win

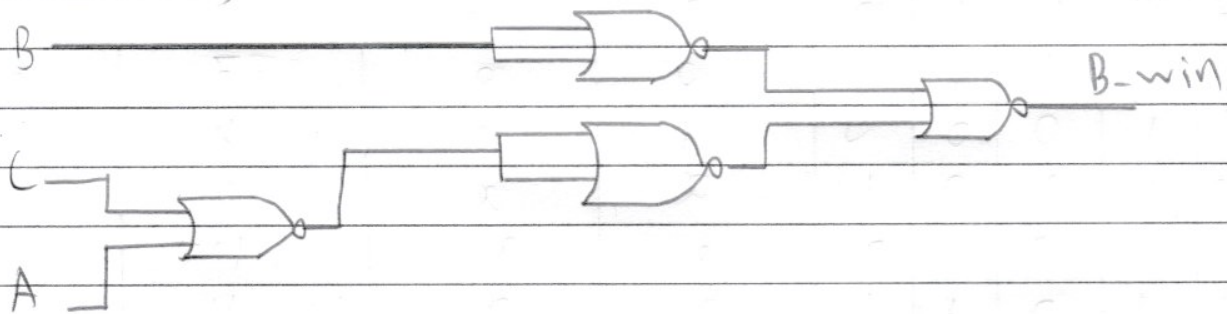

Regarding Alternate B-win solution

$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$	$\bar{A}\bar{C}$	$\bar{A}C$
$\bar{D}$	$\bar{B}$	$\bar{B}$	$BA$	$BA$	$BA$
$\bar{D}$	$\bar{C}$	$\bar{C}$	$0$	$0$	$1$
$\bar{D}$	$\bar{C}$	$0$	$0$	$0$	$0$
$\bar{D}$	$\bar{C}$	$\bar{C}$	$\bar{C}$	$\bar{C}$	$\bar{C}$
$\bar{D}$	$0$	$\bar{C}$	$\bar{C}$	$\bar{C}$	$\bar{C}$

$B\_win = \bar{A}\bar{D}\bar{C}$  cannot be used as B-win lights up on both 0000 and 0010. It also cannot be simplified to compensate for this issue